

Project 1

Problem 1: (This problem is not related to SystemVerilog)

Design a sequential circuit S1 with the following requirements

- The combinational logic part for the next state function should contain at least 3 NAND gates, 2 XOR gates and 2 OR gates.
- The number of the flip-flops should be at least 4.
- The sequential circuit should have at least an output.
- Make sure that your design be different from those used by other students. If your design is identical to a design used by other students, you will be asked to revise your design and redo the work.

Instructions for Problem 1:

- Draw your sequential circuit S1.
- Create the next state function table for S1.
- Draw the state transition graph of S1 including all the POSSIBLE states.
- Figures should be plotted by using a professional software tool. Scanned or cut/paste hand drawn figures and writing are not acceptable.

Problem 2:

- Write the SV code for a 2^n to n priority encoder in the dataflow model (continuous assignments)
- Write the SV code for a 2^n to n priority encoder in the algorithmic model (always_comb).

Problem 3:

- Write the SV code for a 16-bit carry look ahead adder in the dataflow model (continuous assignments)
- Write the SV code for a 16-bit carry look ahead adder in the algorithmic model (always_comb).

Problem 4:

- Write the SV code for a circuit whose 32-bit output is formed by shifting its 32-bit input three positions to the right and filling the vacant positions with the bit that was in the MSB before the shift occurred (shift arithmetic right).
- Write the SV code for a circuit whose 32-bit output is formed by shifting its 32-bit input three positions to the left and filling the vacant positions with 0 (shift logical left).

Problem 5:

- Write the SV code for a 6-bit Binary-to-Gray code converter in the dataflow model (continuous assign)
- Write the SV code for a 6-bit Gray-to-Binary code converter in the algorithmic model (always_comb).

Problem 6: A comparator is a logic macro circuit that compares the magnitude of two n -bit binary operands. A 16-bit comparator determines if a 16-bit vector $a[15:0]$ is equal to a 16-bit vector $b[15:0]$.

- Write the SV code for a 16-bit comparator in the dataflow model (continuous assignments)
- Write the SV code for a 16-bit comparator in the algorithmic model (always_comb).

Project Instructions for Problems 2-6:

- For each design, verify its correctness using your testbench with a simulator.
- You should use the new SV statements instead of the old Verilog statements.
- Turn in your report and code to the D2L by the deadline.
- Your report must contain at least:
 - The SV code with the legible results from the testbench
 - Your code should be packaged and organized with the related task names.
- Only one report is needed for each group. Indicate your email on the first page of your report.